

B.Tech III Year I Semester (R20) Supplementary Examinations August 2023

**MEASUREMENTS & SENSORS**

(Electrical &amp; Electronics Engineering)

Time: 3 hours

Max. Marks: 70

**PART – A**  
(Compulsory Question)

\*\*\*\*\*

1 Answer the following: (10 X 02 = 20 Marks)

- |   |    |
|---|----|
| (a) Define precision.                       | 2M |
| (b) Explain resolution.                     | 2M |
| (c) Write expression for deflecting torque. | 2M |
| (d) Explain driving torque.                 | 2M |
| (e) Discuss working of current transformer. | 2M |
| (f) Explain standardization.                | 2M |
| (g) Draw circuit for Adersons's bridge.     | 2M |
| (h) Explain how to measure loss angle.      | 2M |
| (i) Discuss working of pressure sensor.     | 2M |
| (j) Explain working of motion sensor.       | 2M |

**PART – B**

(Answer all the questions: 05 X 10 = 50 Marks)

- |    |   |     |
|----|---|-----|
| 2  | Discuss working of PMMC and dynamometer instruments.                | 10M |
|    | <b>OR</b>   |     |
| 3  | Explain successive approximation method.                            | 10M |
| 4  | Explain working of dynamometer type PF meter.                       | 10M |
|    | <b>OR</b>   |     |
| 5  | Discuss working of a three phase energy meter.                      | 10M |
| 6  | Explain working of AC potentiometer.                                | 10M |
|    | <b>OR</b>   |     |
| 7  | Elucidate iron loss of bar sample.                                  | 10M |
| 8  | Explain sensitivity of Wheatstone's bridge.                         | 10M |
|    | <b>OR</b>   |     |
| 9  | Discuss measurement of low resistance using Kelvin's double bridge. | 10M |
| 10 | Discuss working of Cathode Ray Tube.                                | 10M |
|    | <b>OR</b>   |     |
| 11 | Explain functionalities horizontal and vertical amplifiers.         | 10M |

\*\*\*\*\*

B.Tech III Year I Semester (R20) Regular &amp; Supplementary Examinations January 2024

**MEASUREMENTS & SENSORS**

(Electrical &amp; Electronics Engineering)

Time: 3 hours

Max. Marks: 70

**PART – A**  
(Compulsory Question)

\*\*\*\*\*

- 1 Answer the following: (10 X 02 = 20 Marks)
- |  |    |
|--|----|
| (a) What is transfer instrument?   | 2M |
| (b) What are the essential parts of the ramp type DVM?   | 2M |
| (c) What is the major cause of creeping error in an energy meter?  | 2M |
| (d) A 3 $\phi$ 500 V motor load has a power factor of 0.4. Two watt meters connected to measure the input. They show the input to be 30 kW. Find the reading of each instrument. | 2M |
| (e) State the advantages of instrument transformers.   | 2M |
| (f) Differentiate the principle of dc potentiometer and ac potentiometer.  | 2M |
| (g) Why Maxwell Bridge is limited to the measurement of medium – Q coils?  | 2M |
| (h) What are the methods of measurements of medium resistance?   | 2M |
| (i) List out the applications of CRO's.  | 2M |
| (j) What is meant by recurrent sweep in cathode ray tube?  | 2M |

**PART – B**

(Answer all the questions: 05 X 10 = 50 Marks)

- 2 How is the current range of PMMC instrument extended with the help of shunt & voltmeter range extended with the help of multiplier? 10M

**OR**

- 3 Explain the working of Digital Frequency meter in detail. 10M

- 4 (a) With a neat sketch explain the construction and working of electro-dynamometer type single phase power factor meter. 6M
- (b) Two wattmeters are connected to measure the power consumed by a 3-phase load with power factor 0.4. Total power consumed by the load, as indicated by the two wattmeters is 30 kW. Find the individual wattmeter readings. 4M

**OR**

- 5 Derive an expression for the driving torque in a single phase induction type meter. Show that the driving torque is maximum when the phase angle between the two fluxes is 90° and the rotating disc is purely non-inductive. 10M

- 6 A current transformer with bar primary has 300 turns in its secondary winding. The resistance and reactance of the secondary circuit are 1.5  $\Omega$  and 1.0  $\Omega$  respectively, including the transformer winding. With 5A flowing in the secondary winding, the magnetizing mmf is 100AT and the core loss is 1.2 W. Determine the ratio and phase angle errors. 10M

**OR**

- 7 Describe the method of determination of BH curve of magnetic material using Method of Reversals. 10M

Contd. in Page 2

- 8 (a) Write briefly on measurement of high resistance by loss of charge method. List the precautions in this method. 7M  
(b) What are the difficulties in measurement of high resistance? 3M

**OR**

- 9 Sketch the circuit diagram of Anderson's bridge. Derive the equations for resistive and inductive components of the inductor to be measured. 10M
- 10 (a) The deflection sensitivity of an oscilloscope is 35 V/cm. If the distance from the deflection plates to the CRT screen is 16 cm, the length of the deflection plates is 2.5 cm and the distance between the deflection plates is 1.2 cm, what is the acceleration anode voltage? 6M  
(b) Write a short note on vertical amplifier. 4M

**OR**

- 11 Explain the working principle of a Linear Variable Differential Transformer (LVDT). Show how it can be used for measuring small mechanical displacements. 10M

\*\*\*\*\*