


TWO PORT NETWORKS

Port :-


A pair of terminals at which electrical signal may enter or leave the network is called "Port."

One Port Network :- A Network having only one pair of terminals is called "One Port Network."

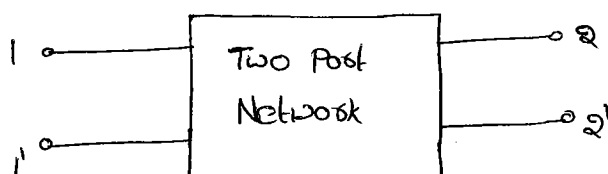Two Port Network :- A Network having two pairs of terminals is called "Two Port Network."



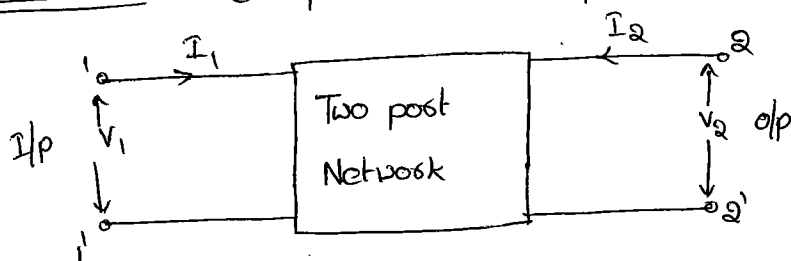Z-Parameters (Impedance or Open Circuit Parameters) :-



Here V_1, V_2 are dependent variables and I_1, I_2 are independent variables.

\therefore Z-Parameters equations are

$$V_1 = Z_{11} I_1 + Z_{12} I_2 \quad \text{--- ①}$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 \quad \text{--- ②}$$

$Z_{11}, Z_{12}, Z_{21}, Z_{22}$ are called Impedance parameters.

Matrix Representation:

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$[V] = [Z] [I]$$

To obtain Z_{11} and Z_{21} , Open Circuit Port '2' i.e, $I_2 = 0$

\therefore From eqn ①, $V_1 = Z_{11} I_1$

$$\Rightarrow \boxed{Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0}}$$

$\therefore Z_{11}$ is called "Open Circuit Driving Point input impedance".

From eqn ②, $V_2 = Z_{21} I_1$

$$\Rightarrow \boxed{Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0}}$$

$\therefore Z_{21}$ is called "Open ckt Forward Transfer impedance".

To obtain Z_{12} and Z_{22} parameters, Open ckt port '1' i.e, $I_1 = 0$

\therefore From eqn ①,

$$\boxed{Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0}}$$

$\therefore Z_{12}$ is called "Open Ckt Reverse Transfer impedance".


From eqn ②,

$$\boxed{Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0}}$$

Z_{22} is called "Open Ckt Driving Point output impedance".

The Z-parameters are obtained only when the current in one port is zero i.e., one of the port is open circuited. Hence the Z-parameters are also called "Open Circuit parameters" or "Impedance parameters".

Equivalent Circuit :-

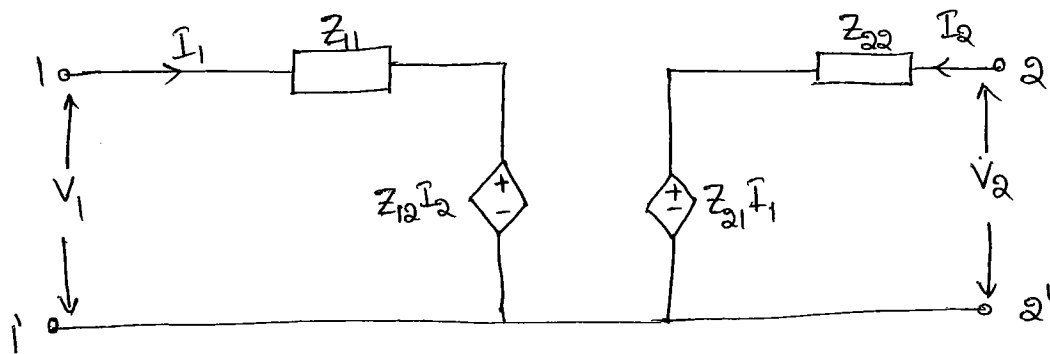

NOTE:-

- If the voltages and currents corresponding to the same ports, then the parameters are called "Driving Point parameters."
- If the voltages or currents corresponding to the different ports, then the parameters are called "Transfer parameters."


Reciprocal Network :- (Reciprocity condition)

When $Z_{12} = Z_{21}$ then network is called "Reciprocal Network."

Symmetrical Network :-

When $Z_{11} = Z_{22}$ then network is called "Symmetrical Network."

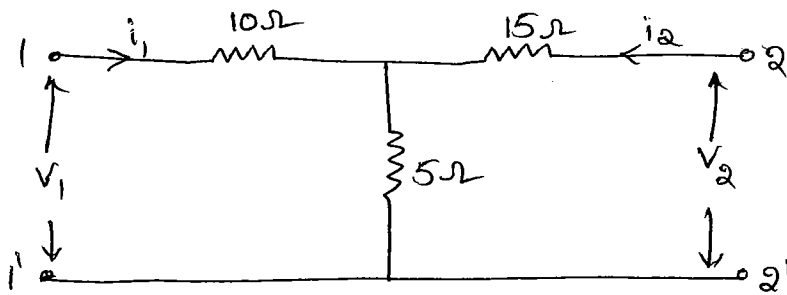→ Find the z-parameters for the given circuit. (T-Network)



Soln

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$


$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0}$$

$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}$$

$$Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0}$$

$$Z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$

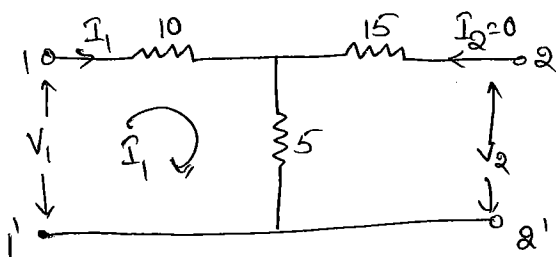To find parameters Z_{11}, Z_{21} open circuit port 2 i.e. $I_2 = 0$




$$V_1 = 10I_1 + 5I_1$$

$$= 15I_1$$

$$\Rightarrow \frac{V_1}{I_1} = 15\Omega = Z_{11}$$

$$V_2 = 5I_1 \Rightarrow \frac{V_2}{I_1} = 5\Omega = Z_{21}$$

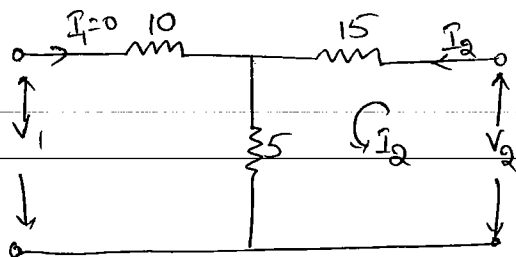To find parameters Z_{12}, Z_{22} open circuit port 1 i.e. $I_1 = 0$



$$V_2 = 15I_2 + 5I_2$$

$$= 20I_2$$


$$\Rightarrow \frac{V_2}{I_2} = 20\Omega = Z_{22}$$

$$V_1 = 5I_2 \Rightarrow \frac{V_1}{I_2} = 5\Omega = Z_{12}$$

$$\therefore \text{z-parameters are } \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} 15 & 5 \\ 5 & 20 \end{bmatrix}$$

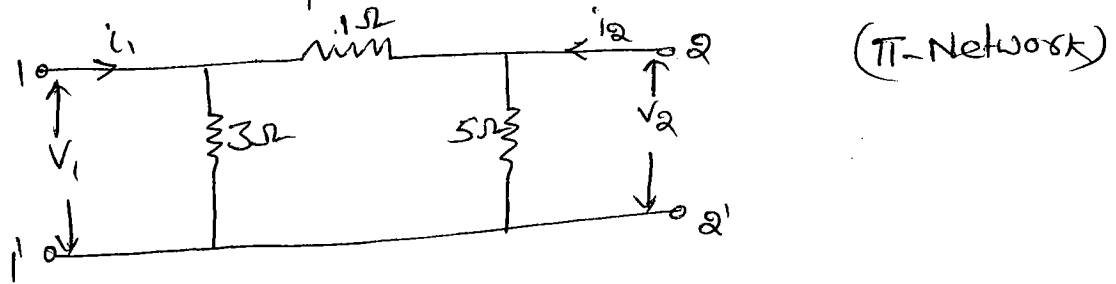
(5)

→ Determine the z-parameters for the given circuit



Sol:-

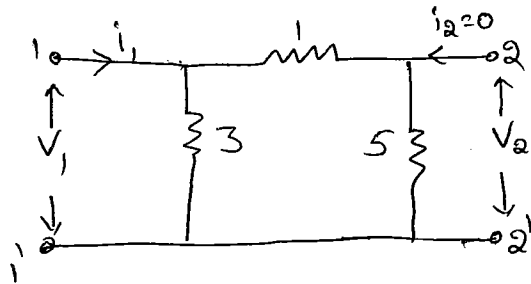To find parameters Z_{11}, Z_{21} Open ckt Port 2 i.e. $I_2 = 0$




$$V_1 = Z_{eq} i_1$$

$$\Rightarrow Z_{eq} = \frac{V_1}{i_1}$$

$$Z_{eq} = R_{eq} = (1+5) \parallel 3 = \frac{3 \times 6}{9} = \underline{\underline{2 \Omega}}$$

$$\therefore Z_{11} = \frac{V_1}{i_1} = \underline{\underline{2 \Omega}}$$

$$Z_{21} = \left. \frac{V_2}{i_1} \right|_{i_2=0}$$

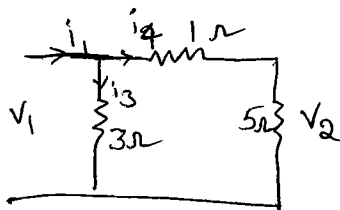


$$V_2 = 5 i_4$$

$$= 5 \times \frac{3}{3+5+1} i_1 = \frac{15}{9} i_1 = \frac{5}{3} i_1$$

$$Z_{21} = \frac{V_2}{i_1} = \underline{\underline{\frac{5}{3} \Omega}}$$

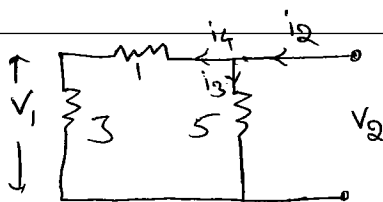To find parameters Z_{12}, Z_{22} Open ckt port 1 i.e. $I_1 = 0$



$$Z_{eq} = (1+3) \parallel 5 = \frac{5 \times 4}{9} = \frac{20}{9} \Omega$$

$$V_2 = Z_{eq} i_2$$

$$\Rightarrow Z_{22} = Z_{eq} = \frac{V_2}{i_2} = \underline{\underline{\frac{20}{9} \Omega}}$$

(6)


$$V_1 = 3 \times I_4 = 3 \times \frac{5 I_2}{3+5+1} = \frac{15}{9} I_2$$

$$\Rightarrow Z_{12} = \frac{V_1}{I_2} = \underline{\underline{\frac{5}{3} \Omega}}$$

$$\therefore Z\text{-parameters are } \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} 2 & 5/3 \\ 5/3 & 20/9 \end{bmatrix}$$

$Z_{12} = Z_{21} \Rightarrow$ The given n/p is Reciprocal Network

Y-Parameters (Admittance Parameters):-

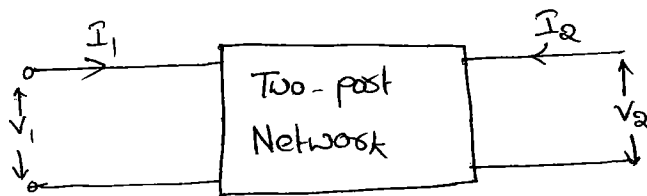

Here I_1, I_2 are dependent variables and V_1, V_2 are independent variables.

$$\therefore I_1 = f(V_1, V_2)$$

$$I_2 = f(V_1, V_2)$$

$$I_1 = Y_{11} V_1 + Y_{12} V_2 \quad \text{--- ①}$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2 \quad \text{--- ②}$$

Here $Y_{11}, Y_{12}, Y_{21}, Y_{22}$ are the admittance parameters

$$\therefore Y = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix}$$

To obtain Y_{11}, Y_{21} parameters short ckt port '2' i.e. $V_2 = 0$

$$\therefore \text{①} \Rightarrow I_1 = Y_{11} V_1 \Rightarrow \boxed{Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0}}$$

Here Y_{11} is called Short ckt Driving point i/p admittance

$$\textcircled{2} \Rightarrow \bar{I}_2 = Y_{21} V_1$$

$$Y_{21} = \left. \frac{\bar{I}_2}{V_1} \right|_{V_2=0}$$

Here Y_{21} is called "Short ckt forward Transfer admittance".

To obtain Y_{12}, Y_{22} parameters short ckt port-1 i.e. $V_1 = 0$

$$\therefore \textcircled{1} \Rightarrow \bar{I}_1 = Y_{12} V_2 \Rightarrow Y_{12} = \left. \frac{\bar{I}_1}{V_2} \right|_{V_1=0}$$


Here Y_{12} is called "Short ckt reverse transfer admittance".

$$\textcircled{2} \Rightarrow \bar{I}_2 = Y_{22} V_2 \Rightarrow Y_{22} = \left. \frac{\bar{I}_2}{V_2} \right|_{V_1=0}$$

Here Y_{22} is called "Short ckt Driving point o/p admittance".

\therefore In order to determine Y-parameters, the voltage in any of the port must become zero i.e. short circuited. Hence Y-parameters are also called "Short ckt parameters".

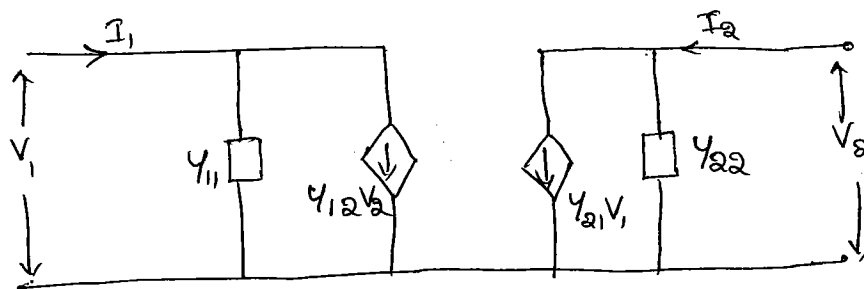
The equivalent ckt representing the Y-parameters is shown below:




Reciprocal condition is $Y_{12} = Y_{21}$

Symmetrical condition is $Y_{11} = Y_{22}$

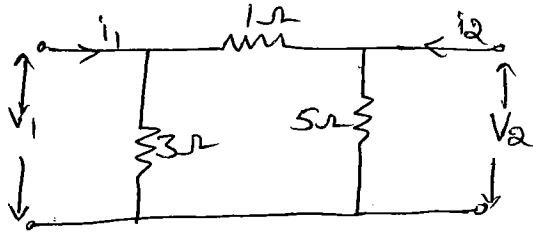→ Determine Y-parameters for the given circuit.



Sol:- Port '2' is short circuited

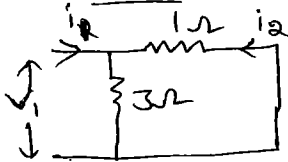

$$Z_{eq} = 3 \parallel 1 = \frac{3}{4} \Omega$$


$$Y_{eq} = \frac{4}{3} \text{ S}$$

$$I_1 = Y_{11} V_1 \Rightarrow Y_{11} = \frac{I_1}{V_1} = \underline{\underline{\frac{4}{3} \text{ S}}}$$

$$I_2 = -\frac{3}{4} i_1, \quad V_1 = \frac{3}{4} i_1$$

$$\therefore Y_{21} = \frac{I_2}{V_1} = \frac{-3/4 i_1}{3/4 i_1} = \underline{\underline{-1 \text{ S}}}$$

Port '1' is short circuited

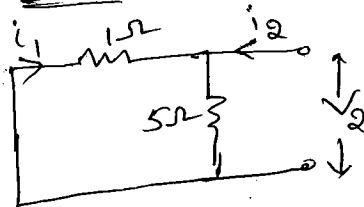

$$Z_{eq} = 1 \parallel 5 = \frac{5}{6} \Omega$$

$$I_2 = Y_{22} V_2 \Rightarrow Y_{22} = \frac{I_2}{V_2} = \underline{\underline{\frac{6}{5} \text{ S}}}$$

$$i_1 = -\frac{5}{6} i_2, \quad V_2 = \frac{5}{6} i_2$$

$$\therefore \frac{i_1}{V_2} = -1 = Y_{12}$$

$$\therefore \text{Y-parameters} \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} 4/3 & -1 \\ -1 & 6/5 \end{bmatrix}$$

Hence this is Reciprocal Network

Alternate Method:-

$$Y = \frac{1}{Z} = Z^{-1}$$

$$Y = \begin{bmatrix} 2 & 5/3 \\ 5/3 & 20/9 \end{bmatrix}^{-1}$$


$$A^{-1} = \frac{1}{ad-bc} \begin{bmatrix} d & -b \\ -c & a \end{bmatrix}$$

$$= \frac{1}{\frac{40}{9} - \frac{25}{9}} \begin{bmatrix} 20/9 & -5/3 \\ -5/3 & 2 \end{bmatrix}$$

$$= \frac{9}{15} \begin{bmatrix} 20/9 & -5/3 \\ -5/3 & 2 \end{bmatrix} = \underline{\underline{\begin{bmatrix} 4/3 & -1 \\ -1 & 6/5 \end{bmatrix}}}$$

ABCD (or) Transmission Parameters:-

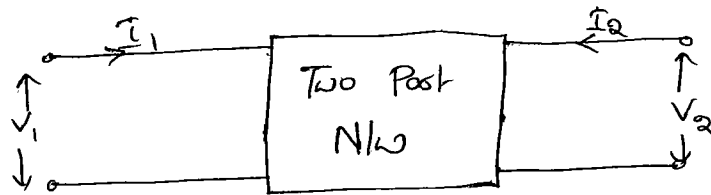These are generally used in the analysis of transmission in which input port is referred as Sending end and output port is referred as Receiving End.



Characteristic eq's:- $V_1 = AV_2 - BI_2$ — ①

$I_1 = CV_2 - DI_2$ — ②

Where A, B, C, D are called Chain (or) Transmission Parameters.

∴ To obtain parameters A, c open ckt port '2' i.e. $I_2 = 0$

$$\therefore \text{①} \Rightarrow \boxed{A = \frac{V_1}{V_2} \Big|_{I_2=0}}$$

A is called "Open ckt reverse voltage gain".

② \Rightarrow

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0}$$

'C' is called open circuit transfer admittance."

ii. To obtain the parameters B, D Short ckt port '2' i.e. $V_2 = 0$

$$① \Rightarrow B = \left. -\frac{V_1}{I_2} \right|_{V_2=0}$$

'B' is called "Short circuit transfer impedance."


$$② \Rightarrow D = \left. -\frac{I_1}{I_2} \right|_{V_2=0}$$

'D' is called "Short ckt Reverse Current gain."


For symmetrical Network $A = D$

For Reciprocal Network $AD - BC = 1$

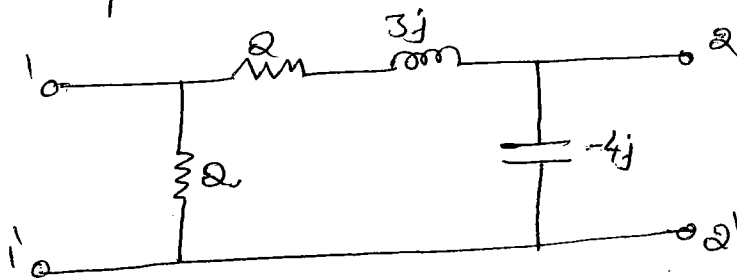→ Verify whether the given n/w is reciprocal or not using ABCD parameters.



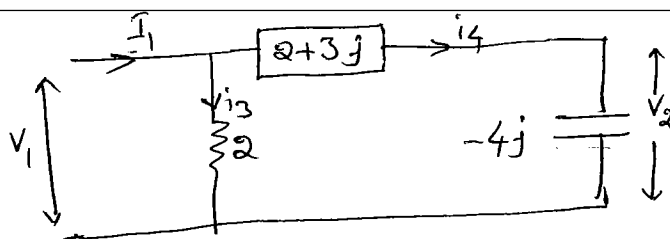Sol: Case (i): Open ckt o/p port $I_2 = 0$



$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0}$$

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0}$$

$$V_2 = I_4 (-4j) = \frac{2}{2+2+3j-4j} \times I_1 (-4j) = \frac{-8j I_1}{4-j}$$


$$Z_{eq} = (2+3j-4j) \parallel 2 = \frac{(2-j)2}{2-j+2} = \frac{4-2j}{4-j} = 1.05 - 0.23j$$

$$V_1 = \bar{I}_1 Z_{eq} = (1.05 - 0.23j) \bar{I}_1$$

$$A = \frac{V_1}{V_2} = \frac{(1.05 - 0.23j) \bar{I}_1}{-8j \bar{I}_1} \times (4-j) = \underline{\underline{0.24 + 0.525j}}$$

$$C = \frac{\bar{I}_1}{V_2} = \frac{4-j}{-8j} = \underline{\underline{0.125 + 0.5j}}$$

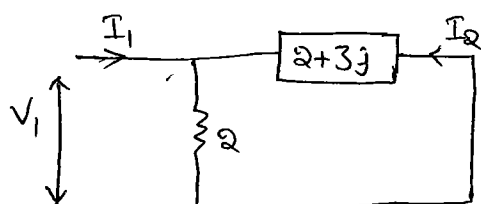case(ii) :- Short ckt o/p port, $V_2 = 0$



$$B = \left. \frac{-V_1}{\bar{I}_2} \right|_{V_2=0}$$

$$D = \left. \frac{-\bar{I}_1}{\bar{I}_2} \right|_{V_2=0}$$

$$Z_{eq} = \frac{2 \times (2+3j)}{2+2+3j} = \underline{\underline{1.36 + 0.48j}}$$

$$V_1 = Z_{eq} \bar{I}_1 = (1.36 + 0.48j) \bar{I}_1$$

$$\bar{I}_2 = -\frac{2}{2+3j+2} \bar{I}_1 = \frac{-2}{4+3j} \bar{I}_1$$

$$\therefore B = \frac{-V_1}{\bar{I}_2} = \frac{-(1.36 + 0.48j) \bar{I}_1}{-2 \bar{I}_1} \times (4+3j) = \underline{\underline{2.72 + 2.46j}}$$


$$D = \frac{-\bar{I}_1}{\bar{I}_2} = \frac{4+3j}{2} = \underline{\underline{2 + 1.5j}}$$

$$\begin{aligned} AD - BC &= (0.24 + 0.525j)(2 + 1.5j) - (2.72 + 2.46j)(2 + 1.5j) \\ &= \underline{\underline{-2.057 - 7.59j}} \neq 1 \end{aligned}$$

\therefore The given network is not reciprocal network

Hybrid Parameters:- (H-Parameters)

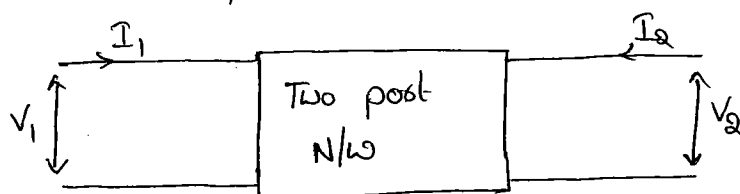H-parameter representation is used in modelling of electronic components & circuits, particularly transistors.



$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

$$V_1 = h_{11} I_1 + h_{12} V_2 \quad \text{--- (1)}$$

$$I_2 = h_{21} I_1 + h_{22} V_2 \quad \text{--- (2)}$$

Case (i):- To obtain the parameters h_{11} , h_{21} short ckt port (2) i.e. $V_2 = 0$.

$$\textcircled{1} \Rightarrow h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0} \Omega$$

h_{11} is called "Short ckt driving point i/p impedance."

$$\textcircled{2} \Rightarrow h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0}$$

h_{21} is called "Short ckt forward current gain."

Case (ii):- To obtain the parameters h_{12} , h_{22} open ckt port (1) i.e. $I_1 = 0$


$$\textcircled{1} \Rightarrow h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0}$$

h_{12} is called "Open ckt reverse voltage gain."

$$\textcircled{2} \Rightarrow h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0} (\Omega)$$

h_{22} is called "Open ckt driving point o/p admittance."

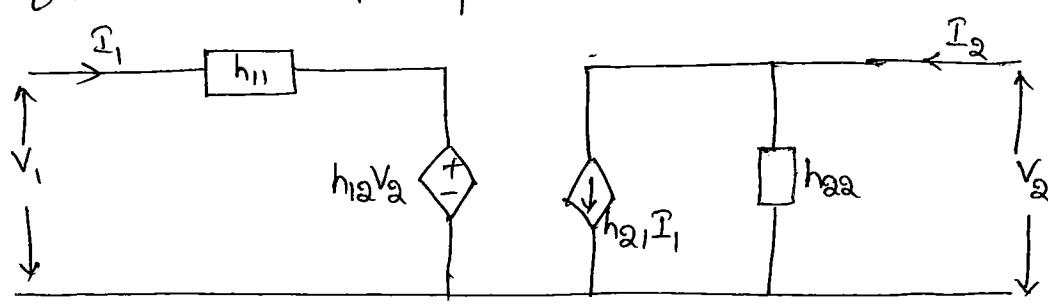The equivalent ckt of h-parameters is shown below:




Reciprocal condition:- $h_{12} = -h_{21}$


Symmetrical condition:- $\Delta h = 1$

$$h_{11}h_{22} - h_{12}h_{21} = 1$$

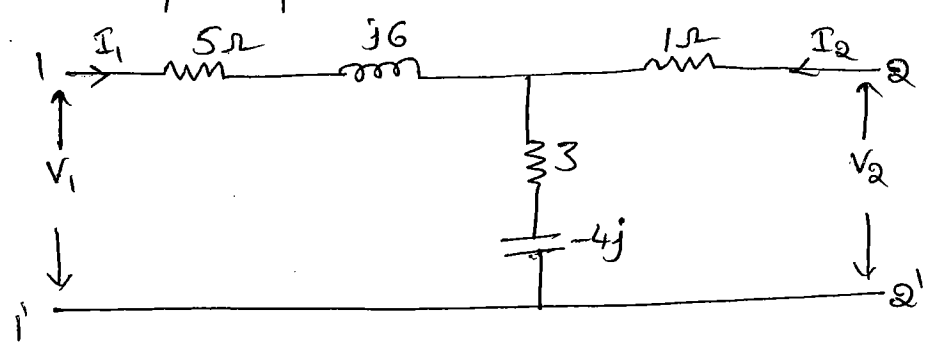→ Obtain hybrid parameters for the given network :-



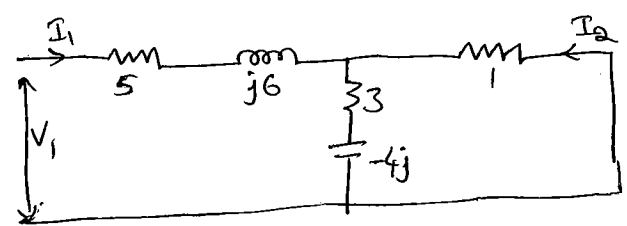Sol:- case(i):- Short ckt o/p port $V_2 = 0$



$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0} \quad h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0}$$

$$Z_{eq} = [1 \parallel (3-4j)] + 5 + j6 = \frac{3-4j}{4-4j} + 5 + 6j$$

$$= 5.875 + 5.875j$$


$$V_1 = Z_{eq} I_1 = (5.875 + 5.875j) I_1 \quad \text{--- ①}$$

$$I_2 = - \frac{(3-4j)}{3-4j+1} I_1 = (0.875 - 0.125j) I_1 \quad \text{--- ②}$$

$$\text{①} \Rightarrow h_{11} = \frac{V_1}{I_1} = \underline{\underline{5.875 + 5.875j}}$$

$$\textcircled{2} \Rightarrow h_{21} = \frac{I_2}{I_1} = \underline{\underline{0.875 - 0.125j}}$$

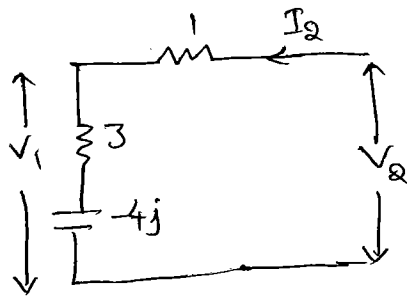Case (ii):- Open ckt the input port, $I_1 = 0$



$$h_{12} = \frac{V_1}{V_2} \Big|_{I_1=0} \quad h_{22} = \frac{I_2}{V_2} \Big|_{I_1=0}$$

$$Z_{eq} = 1 + 3 - 4j = 4 - 4j$$

$$V_2 = I_2 Z_{eq} = (4 - 4j) I_2 \text{ --- } \textcircled{3}$$

$$V_1 = \frac{3 - 4j}{3 - 4j + 1} V_2 = \frac{3 - 4j}{4 - 4j} V_2 \text{ --- } \textcircled{4}$$

$$\textcircled{3} \Rightarrow h_{22} = \frac{I_2}{V_2} = \frac{1}{4 - 4j} = \underline{\underline{0.125 + 0.125j}}$$

$$\textcircled{4} \Rightarrow h_{12} = \frac{V_1}{V_2} = \frac{3 - 4j}{4 - 4j} = \underline{\underline{0.875 - 0.125j}}$$

Relationship between parameters:-

i. Z-parameters in terms of Y-parameters:-

$$Z = [Y]^{-1} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix}^{-1}$$

$$= \frac{1}{Y_{11}Y_{22} - Y_{21}Y_{12}} \begin{bmatrix} Y_{22} & -Y_{12} \\ -Y_{21} & Y_{11} \end{bmatrix} = \begin{bmatrix} \frac{Y_{22}}{\Delta Y} & \frac{-Y_{12}}{\Delta Y} \\ \frac{-Y_{21}}{\Delta Y} & \frac{Y_{11}}{\Delta Y} \end{bmatrix}$$

$$\therefore \begin{aligned} Z_{11} &= \frac{Y_{22}}{\Delta Y} & Z_{12} &= \frac{-Y_{12}}{\Delta Y} \\ Z_{21} &= \frac{-Y_{21}}{\Delta Y} & Z_{22} &= \frac{Y_{11}}{\Delta Y} \end{aligned}$$

2. Z in terms of ABCD parameters :-

We know, $V_1 = Z_{11} I_1 + Z_{12} I_2$ — ① (V_1, I_1, I_2)

$$V_2 = Z_{21} I_1 + Z_{22} I_2 \text{ — ② } (V_2, I_1, I_2)$$

For ABCD parameters,

$$V_1 = A V_2 - B I_2 \text{ — ③ } (V_1, V_2, I_2)$$

$$I_1 = C V_2 - D I_2 \text{ — ④ } (I_1, V_2, I_2)$$

From eqn ④ $\Rightarrow V_2 = \frac{I_1 + D I_2}{C} = \frac{I_1}{C} + \frac{D}{C} I_2$ — ⑤

Compare ⑤ with ②

$$\Rightarrow \boxed{Z_{21} = \frac{1}{C}, \quad Z_{22} = \frac{D}{C}}$$

Substitute ⑤ in ③,

$$\begin{aligned} V_1 &= A \left[\frac{I_1}{C} + \frac{D}{C} I_2 \right] - B I_2 \\ &= \frac{A}{C} I_1 + \left(\frac{AD}{C} - B \right) I_2 \text{ — ⑥} \end{aligned}$$

Compare ⑥ with ①

$$\Rightarrow \boxed{Z_{11} = \frac{A}{C}, \quad Z_{12} = \frac{AD - BC}{C}}$$

3. Z in terms of H parameters :-

We know, $V_1 = Z_{11} I_1 + Z_{12} I_2$ — ① (V_1, I_1, I_2)

$$V_2 = Z_{21} I_1 + Z_{22} I_2 \text{ — ② } (V_2, I_1, I_2)$$

For h-parameters,

$$V_1 = h_{11} I_1 + h_{12} V_2 \text{ — ③ } (V_1, I_1, V_2)$$

$$I_2 = h_{21} I_1 + h_{22} V_2 \text{ — ④ } (I_2, I_1, V_2)$$

From eqn ④ $\Rightarrow h_{22} V_2 = I_2 - h_{21} I_1$

$$V_2 = \frac{1}{h_{22}} I_2 - \frac{h_{21}}{h_{22}} I_1$$

$$= -\left(\frac{h_{21}}{h_{22}}\right) I_1 + \frac{1}{h_{22}} I_2 \text{ --- ⑤}$$

Compare ⑤ with ②

$$\Rightarrow Z_{21} = -\frac{h_{21}}{h_{22}}, \quad Z_{22} = \frac{1}{h_{22}}$$

Substitute ⑤ in ③

$$\begin{aligned} \Rightarrow V_1 &= h_{11} I_1 + h_{12} \left[-\frac{h_{21}}{h_{22}} I_1 + \frac{1}{h_{22}} I_2 \right] \\ &= \frac{h_{11} h_{22} - h_{12} h_{21}}{h_{22}} I_1 + \frac{h_{12}}{h_{22}} I_2 \text{ --- ⑥} \end{aligned}$$

From eqns ⑤ & ⑥

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} \frac{h_{11} h_{22} - h_{12} h_{21}}{h_{22}} & \frac{h_{12}}{h_{22}} \\ -\frac{h_{21}}{h_{22}} & \frac{1}{h_{22}} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

Y-Parameters in terms of other parameters:-

1. Y in terms of Z-parameters:-

The equations representing Y-parameters are

$$I_1 = Y_{11} V_1 + Y_{12} V_2 \text{ --- ① } (I_1, V_1, V_2)$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2 \text{ --- ② } (I_2, V_1, V_2)$$

For Z-parameters, $V_1 = Z_{11} I_1 + Z_{12} I_2 \text{ --- ③ } (V_1, I_1, I_2)$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 \text{ --- ④ } (V_2, I_1, I_2)$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \frac{1}{\Delta} \begin{bmatrix} Z_{22} & -Z_{12} \\ -Z_{21} & Z_{11} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$\text{Where } \Delta = Z_{11}Z_{22} - Z_{12}Z_{21}$$

Q. Y in terms of ABCD parameters:-

$$\text{For Y-parameters, } I_1 = Y_{11}V_1 + Y_{12}V_2 \text{ --- (1) } (I_1, V_1, V_2)$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2 \text{ --- (2) } (I_2, V_1, V_2)$$

$$\text{For ABCD parameters, } V_1 = AV_2 - BI_2 \text{ --- (3) } (V_1, V_2, I_2)$$

$$I_1 = CV_2 - DI_2 \text{ --- (4) } (I_1, V_2, I_2)$$

$$\begin{aligned} \text{From eqn (3)} \Rightarrow I_2 &= \frac{A}{B}V_2 - \frac{1}{B}V_1 \\ &= -\frac{1}{B}V_1 + \frac{A}{B}V_2 \text{ --- (5)} \end{aligned}$$

$$\text{Compare (2) \& (5)} \Rightarrow Y_{21} = -\frac{1}{B} \quad Y_{22} = \frac{A}{B}$$

Substitute eqn (5) in (4)

$$\begin{aligned} \Rightarrow I_1 &= CV_2 - D \left[-\frac{1}{B}V_1 + \frac{A}{B}V_2 \right] \\ &= \frac{D}{B}V_1 + \frac{BC-AD}{B}V_2 \text{ --- (6)} \end{aligned}$$

$$\text{Compare (6) \& (1)} \Rightarrow Y_{11} = \frac{D}{B}, \quad Y_{12} = \frac{BC-AD}{B}$$

$$\therefore \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} \frac{D}{B} & \frac{BC-AD}{B} \\ -\frac{1}{B} & \frac{A}{B} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

3. Y in terms of h-parameters:-

For Y-parameters, $I_1 = Y_{11} V_1 + Y_{12} V_2$ — (1) (I_1, V_1, V_2)

$I_2 = Y_{21} V_1 + Y_{22} V_2$ — (2) (I_2, V_1, V_2)

For h-parameters, $V_1 = h_{11} I_1 + h_{12} V_2$ — (3) (V_1, I_1, V_2)

$I_2 = h_{21} I_1 + h_{22} V_2$ — (4) (I_2, I_1, V_2)

From eqn (3) $\Rightarrow I_1 = \frac{1}{h_{11}} V_1 + \left(-\frac{h_{12}}{h_{11}}\right) V_2$ — (5)

Substitute eqn (5) in eqn (4)

$$\begin{aligned} \Rightarrow I_2 &= h_{21} \left[\frac{1}{h_{11}} V_1 - \frac{h_{12}}{h_{11}} V_2 \right] + h_{22} V_2 \\ &= \frac{h_{21}}{h_{11}} V_1 + \frac{h_{11} h_{22} - h_{12} h_{21}}{h_{11}} V_2 \end{aligned} \quad \text{--- (6)}$$

From eqns (5) & (6)

$$\Rightarrow \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} \frac{1}{h_{11}} & -\frac{h_{12}}{h_{11}} \\ \frac{h_{21}}{h_{11}} & \frac{h_{11} h_{22} - h_{12} h_{21}}{h_{11}} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

ABCD parameters in terms of other parameters:-

1. ABCD in terms of Z-parameters:-

For ABCD parameters, $V_1 = A V_2 - B I_2$ — (1) (V_1, V_2, I_2)

$I_1 = C V_2 - D I_2$ — (2) (I_1, V_2, I_2)

For Z parameters, $V_1 = Z_{11} I_1 + Z_{12} I_2$ — (3) (V_1, I_1, I_2)

$V_2 = Z_{21} I_1 + Z_{22} I_2$ — (4) (V_2, I_1, I_2)

From eqn (4), $z_{21} I_1 = V_2 - z_{22} I_2$

$$\Rightarrow I_1 = \frac{1}{z_{21}} V_2 - \frac{z_{22}}{z_{21}} I_2 \quad \text{--- (5)}$$

Substitute eqn. (5) in equation (3)

$$\begin{aligned} \Rightarrow V_1 &= z_{11} \left[\frac{1}{z_{21}} V_2 - \frac{z_{22}}{z_{21}} I_2 \right] + z_{12} I_2 \\ &= \frac{z_{11}}{z_{21}} V_2 - \frac{z_{22} z_{11} - z_{12} z_{21}}{z_{21}} I_2 \quad \text{--- (6)} \end{aligned}$$

From eqn's (5) & (6)

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} \frac{z_{11}}{z_{21}} & \frac{z_{22} z_{11} - z_{12} z_{21}}{z_{21}} \\ \frac{1}{z_{21}} & \frac{z_{22}}{z_{21}} \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

2. ABCD in terms of Y-parameters:-

For ABCD parameters, $V_1 = A V_2 - B I_2$ --- (1) (V_1, V_2, I_2)

$I_1 = C V_2 - D I_2$ --- (2) (I_1, V_2, I_2)

For Y-parameters, $I_1 = Y_{11} V_1 + Y_{12} V_2$ --- (3) (I_1, V_1, V_2)

$I_2 = Y_{21} V_1 + Y_{22} V_2$ --- (4) (I_2, V_1, V_2)

From eqn (4), $Y_{21} V_1 = -Y_{22} V_2 + I_2$

$$\Rightarrow V_1 = \frac{-Y_{22}}{Y_{21}} V_2 + \frac{1}{Y_{21}} I_2 \quad \text{--- (5)}$$

Substitute eqn. (5) in (3)

$$\Rightarrow I_1 = Y_{11} \left[\frac{-Y_{22}}{Y_{21}} V_2 + \frac{1}{Y_{21}} I_2 \right] + Y_{12} V_2$$

$$= - \left(\frac{Y_{11} Y_{22} - Y_{12} Y_{21}}{Y_{21}} \right) V_2 - \left(-\frac{Y_{11}}{Y_{21}} \right) I_2 \quad \text{--- (6)}$$

From equations ⑤ & ⑥

$$\Rightarrow \begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} -\frac{Y_{22}}{Y_{21}} & -\frac{1}{Y_{21}} \\ -\frac{(Y_{11}Y_{22} - Y_{12}Y_{21})}{Y_{21}} & -\frac{Y_{11}}{Y_{21}} \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

3. ABCD in terms of h-parameters:-

For ABCD parameters, $V_1 = AV_2 - BI_2$ — ① (V_1, V_2, I_2)

$I_1 = CV_2 - DI_2$ — ② (I_1, V_2, I_2)

For h-parameters, $V_1 = h_{11}I_1 + h_{12}V_2$ — ③ (V_1, I_1, V_2)

$I_2 = h_{21}I_1 + h_{22}V_2$ — ④ (I_2, I_1, V_2)

From eqn ④ $\Rightarrow h_{21}I_1 = -h_{22}V_2 + I_2$

$$I_1 = -\frac{h_{22}}{h_{21}}V_2 - \left(-\frac{1}{h_{21}}\right)I_2 \text{ — ⑤}$$

Substitute eqn ⑤ in ③ $\Rightarrow V_1 = h_{11}\left[-\frac{h_{22}}{h_{21}}V_2 + \frac{1}{h_{21}}I_2\right] + h_{12}V_2$

$$= \frac{-h_{11}h_{22} + h_{12}h_{21}}{h_{21}}V_2 - \left(-\frac{h_{11}}{h_{21}}\right)I_2 \text{ — ⑥}$$

From eqn's ⑤ & ⑥ \Rightarrow

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} \frac{-h_{11}h_{22} + h_{12}h_{21}}{h_{21}} & -\frac{h_{11}}{h_{21}} \\ -\frac{h_{22}}{h_{21}} & -\frac{1}{h_{21}} \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

H-parameters in terms of other parameters:-

1. H in terms of z-parameters:-

For h-parameters, $V_1 = h_{11} I_1 + h_{12} V_2$ — ① (V_1, I_1, V_2)

$I_2 = h_{21} I_1 + h_{22} V_2$ — ② (I_2, I_1, V_2)

For z-parameters, $V_1 = z_{11} I_1 + z_{12} I_2$ — ③ (V_1, I_1, I_2)

$V_2 = z_{21} I_1 + z_{22} I_2$ — ④ (V_2, I_1, I_2)

From eqn ④ $\Rightarrow z_{22} I_2 = -z_{21} I_1 + V_2$

$\Rightarrow I_2 = \frac{-z_{21}}{z_{22}} I_1 + \frac{1}{z_{22}} V_2$ — ⑤

From & substitute eqn ⑤ in eqn ③

$$\begin{aligned} \Rightarrow V_1 &= z_{11} I_1 + z_{12} \left[\frac{-z_{21}}{z_{22}} I_1 + \frac{1}{z_{22}} V_2 \right] \\ &= \frac{z_{11} z_{22} - z_{12} z_{21}}{z_{22}} I_1 + \frac{z_{12}}{z_{22}} V_2 \end{aligned} \quad \text{--- ⑥}$$

From eqn's ⑤ & ⑥

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} \frac{z_{11} z_{22} - z_{12} z_{21}}{z_{22}} & \frac{z_{12}}{z_{22}} \\ -\frac{z_{21}}{z_{22}} & \frac{1}{z_{22}} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

2. H in terms of y-parameters:-

For h-parameters, $V_1 = h_{11} I_1 + h_{12} V_2$ — ① (V_1, I_1, V_2)

$I_2 = h_{21} I_1 + h_{22} V_2$ — ② (I_2, I_1, V_2)

For y-parameters, $I_1 = y_{11} V_1 + y_{12} V_2$ — ③ (I_1, V_1, V_2)

$I_2 = y_{21} V_1 + y_{22} V_2$ — ④ (I_2, V_1, V_2)

$$\therefore \text{From eqn ③} \Rightarrow Y_{11} V_1 = I_1 - Y_{12} V_2$$

$$V_1 = \frac{1}{Y_{11}} I_1 - \frac{Y_{12}}{Y_{11}} V_2 \quad \text{--- ⑤}$$

Substitute eqn ⑤ in eqn ④

$$\begin{aligned} \Rightarrow I_2 &= Y_{21} \left[\frac{1}{Y_{11}} I_1 - \frac{Y_{12}}{Y_{11}} V_2 \right] + Y_{22} V_2 \\ &= \frac{Y_{21}}{Y_{11}} I_1 + \frac{Y_{11} Y_{22} - Y_{21} Y_{12}}{Y_{11}} V_2 \quad \text{--- ⑥} \end{aligned}$$

$$\text{From eqn's ⑤ \& ⑥} \Rightarrow \begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} \frac{1}{Y_{11}} & -\frac{Y_{12}}{Y_{11}} \\ \frac{Y_{21}}{Y_{11}} & \frac{Y_{11} Y_{22} - Y_{21} Y_{12}}{Y_{11}} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

3. h in terms of ABCD parameters:-

$$\text{For h-parameters, } V_1 = h_{11} I_1 + h_{12} V_2 \quad \text{--- ① } (V_1, I_1, V_2)$$

$$I_2 = h_{21} I_1 + h_{22} V_2 \quad \text{--- ② } (I_2, I_1, V_2)$$

$$\text{For ABCD parameters, } V_1 = A V_2 - B I_2 \quad \text{--- ③ } (V_1, V_2, I_2)$$

$$I_1 = C V_2 - D I_2 \quad \text{--- ④ } (I_1, V_2, I_2)$$

$$\text{From eqn ④} \Rightarrow D I_2 = -I_1 + C V_2$$

$$I_2 = \frac{-1}{D} I_1 + \frac{C}{D} V_2 \quad \text{--- ⑤}$$

$$\text{Substitute eqn ⑤ in eqn ③} \Rightarrow V_1 = A V_2 - B \left[\frac{-1}{D} I_1 + \frac{C}{D} V_2 \right]$$

$$\Rightarrow V_1 = \frac{B}{D} I_1 + \frac{AD - BC}{D} V_2 \quad \text{--- ⑥}$$

$$\text{From ⑤ \& ⑥} \Rightarrow \begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} \frac{B}{D} & \frac{AD - BC}{D} \\ \frac{-1}{D} & \frac{C}{D} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

S.No.	Parameter	Dependent Variables	Independent Variables	Equations	Condition for Symmetry	Condition for Reciprocity
1.	Z-parameters (Impedance or) Open ckt parameters	V_1, V_2	I_1, I_2	$V_1 = Z_{11} I_1 + Z_{12} I_2$ $V_2 = Z_{21} I_1 + Z_{22} I_2$	$Z_{11} = Z_{22}$	$Z_{12} = Z_{21}$
2.	Y-parameters (Admittance or) Short ckt parameters	I_1, I_2	V_1, V_2	$I_1 = Y_{11} V_1 + Y_{12} V_2$ $I_2 = Y_{21} V_1 + Y_{22} V_2$	$Y_{11} = Y_{22}$	$Y_{12} = Y_{21}$
3.	ABCD parameters (Chain or) Transmission parameters	V_1, I_1	V_2, I_2	$V_1 = A V_2 - B I_2$ $I_1 = C V_2 - D I_2$	$A = D$	$AD - BC = 1$
4.	H-parameters (Hybrid parameters)	V_1, I_2	V_2, I_1	$V_1 = h_{11} I_1 + h_{12} I_2$ $I_2 = h_{21} I_1 + h_{22} V_2$	$h_{11} h_{22} - h_{12} h_{21} = 1$	$h_{12} = -h_{21}$

Table for Interrelation between various parameters :-

	$[Z]$	$[Y]$	$[h]$	$[T]$
$[Z]$	$\begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix}$	$\begin{bmatrix} \frac{y_{22}}{\Delta Y} & -\frac{y_{12}}{\Delta Y} \\ -\frac{y_{21}}{\Delta Y} & \frac{y_{11}}{\Delta Y} \end{bmatrix}$	$\begin{bmatrix} \frac{\Delta h}{h_{22}} & \frac{h_{12}}{h_{22}} \\ -\frac{h_{21}}{h_{22}} & \frac{1}{h_{22}} \end{bmatrix}$	$\begin{bmatrix} \frac{A}{C} & \frac{\Delta T}{C} \\ \frac{1}{C} & \frac{D}{C} \end{bmatrix}$
$[Y]$	$\begin{bmatrix} \frac{z_{22}}{\Delta Z} & -\frac{z_{12}}{\Delta Z} \\ -\frac{z_{21}}{\Delta Z} & \frac{z_{11}}{\Delta Z} \end{bmatrix}$	$\begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix}$	$\begin{bmatrix} \frac{1}{h_{11}} & -\frac{h_{12}}{h_{11}} \\ \frac{h_{21}}{h_{11}} & \frac{\Delta h}{h_{11}} \end{bmatrix}$	$\begin{bmatrix} \frac{D}{B} & -\frac{\Delta T}{B} \\ -\frac{1}{B} & \frac{A}{B} \end{bmatrix}$
$[h]$	$\begin{bmatrix} \frac{\Delta Z}{z_{22}} & \frac{z_{21}}{z_{22}} \\ -\frac{z_{21}}{z_{22}} & \frac{1}{z_{22}} \end{bmatrix}$	$\begin{bmatrix} \frac{1}{y_{11}} & -\frac{y_{12}}{y_{11}} \\ \frac{y_{21}}{y_{11}} & \frac{\Delta Y}{y_{11}} \end{bmatrix}$	$\begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix}$	$\begin{bmatrix} \frac{B}{D} & \frac{AD-BC}{D} \\ -\frac{1}{D} & \frac{C}{D} \end{bmatrix}$
$[T]$	$\begin{bmatrix} \frac{z_{11}}{z_{21}} & \frac{\Delta Z}{z_{21}} \\ \frac{1}{z_{21}} & \frac{z_{22}}{z_{21}} \end{bmatrix}$	$\begin{bmatrix} -\frac{y_{22}}{y_{21}} & -\frac{1}{y_{21}} \\ -\frac{\Delta Y}{y_{21}} & -\frac{y_{11}}{y_{21}} \end{bmatrix}$	$\begin{bmatrix} -\frac{\Delta h}{h_{21}} & -\frac{h_{11}}{h_{21}} \\ -\frac{h_{22}}{h_{21}} & -\frac{1}{h_{21}} \end{bmatrix}$	$\begin{bmatrix} A & B \\ C & D \end{bmatrix}$

Where,

$$\Delta Z = z_{11} z_{22} - z_{12} z_{21}$$


$$\Delta Y = y_{11} y_{22} - y_{12} y_{21}$$

$$\Delta h = h_{11} h_{22} - h_{12} h_{21}$$

$$\Delta T = AD - BC$$

Parallel Connection of 2-port Networks :-

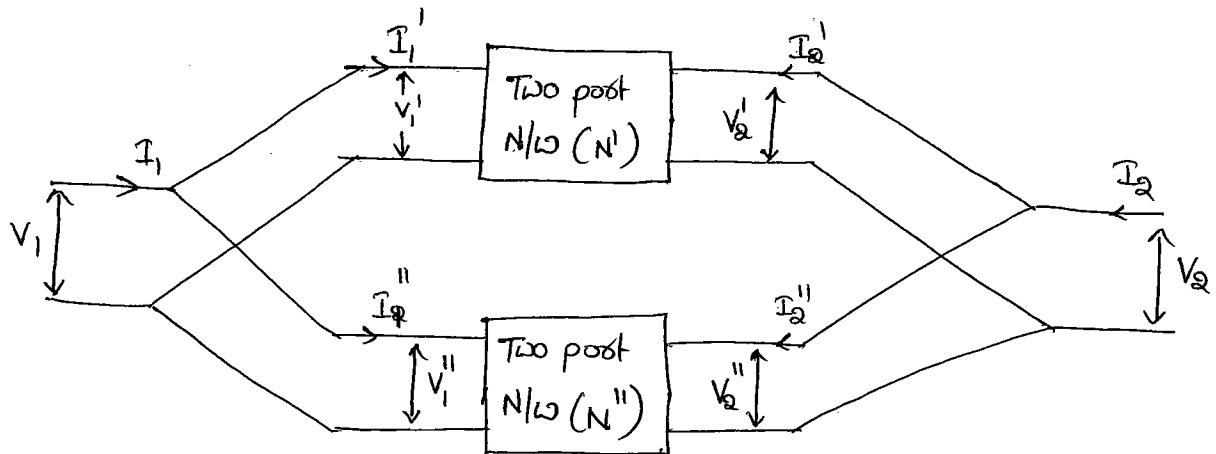Consider two networks N' and N'' are connected in parallel as shown in fig. below. When 2-port Networks are connected in parallel we can add their "y-parameters" to get overall y-parameters of the parallel connection.



Let the y-parameters for the Network N' are $y_{11}', y_{12}', y_{21}', y_{22}'$. Let the y-parameters for the Network N'' are $y_{11}'', y_{12}'', y_{21}'', y_{22}''$. Let the overall y-parameters for parallel connection are $y_{11}, y_{12}, y_{21}, y_{22}$.

For a parallel connected N/w, $V_1 = V_1' = V_1''$

$$V_2 = V_2' = V_2''$$

$$I_1 = I_1' + I_1''$$

$$I_2 = I_2' + I_2''$$

For the N/w N' the eqn's representing y-parameters are,

$$I_1' = y_{11}' V_1' + y_{12}' V_2' \quad \text{--- ①}$$

$$I_2' = y_{21}' V_1' + y_{22}' V_2' \quad \text{--- ②}$$

For the N/w N'' the equations representing y -parameters are;

$$I_1'' = y_{11}'' V_1'' + y_{12}'' V_2'' \quad \text{--- (3)}$$

$$I_2'' = y_{21}'' V_1'' + y_{22}'' V_2'' \quad \text{--- (4)}$$

But we know, $I_1 = I_1' + I_1''$

$$= [y_{11}' V_1' + y_{12}' V_2'] + [y_{11}'' V_1'' + y_{12}'' V_2'']$$

$$= [y_{11}' + y_{11}''] V_1 + [y_{12}' + y_{12}''] V_2 \quad \text{--- (5)} \quad (\because V_1 = V_1' = V_1'' \\ V_2 = V_2' = V_2'')$$

Similarly, $I_2 = I_2' + I_2''$


$$= [y_{21}' V_1' + y_{22}' V_2'] + [y_{21}'' V_1'' + y_{22}'' V_2'']$$

$$= [y_{21}' + y_{21}''] V_1 + [y_{22}' + y_{22}''] V_2 \quad \text{--- (6)}$$

From equations (5) & (6), The overall y -parameters of parallel

Connected N/w's,
$$\begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} = \begin{bmatrix} y_{11}' + y_{11}'' & y_{12}' + y_{12}'' \\ y_{21}' + y_{21}'' & y_{22}' + y_{22}'' \end{bmatrix}$$

Series connection of 2-port N/w's :-

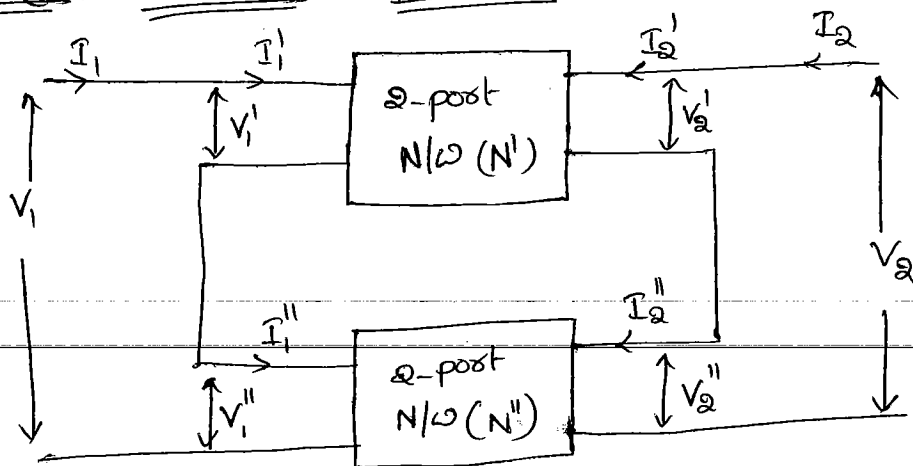

When two ports are connected in series we can add their "z-parameters" to get the overall z -parameters.

Here for series connection, $V_1 = V_1' + V_1''$

$$V_2 = V_2' + V_2''$$

$$I_1 = I_1' + I_1''$$


$$I_2 = I_2' = I_2''$$

$$\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} Z_{11}' + Z_{11}'' & Z_{12}' + Z_{12}'' \\ Z_{21}' + Z_{21}'' & Z_{22}' + Z_{22}'' \end{bmatrix}$$

Cascade Connection of two port Networks:-

The cascade Connection is also called

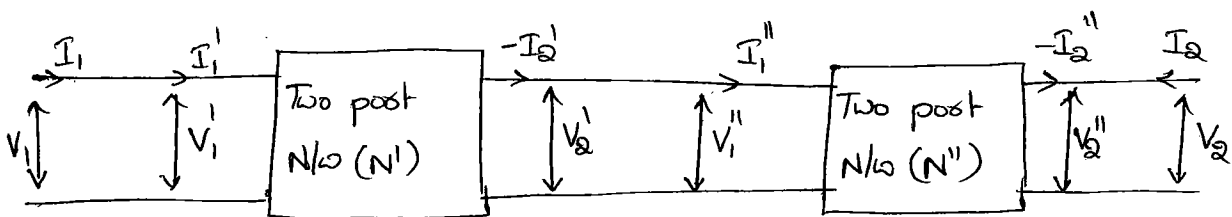"Connection." Consider two Networks N' and N'' are connected in cascade as shown in fig. below: When two ports are connected in cascade, we can multiply their individual transmission parameters to get overall transmission parameters of cascaded connection.



$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} A' & B' \\ C' & D' \end{bmatrix} \begin{bmatrix} A'' & B'' \\ C'' & D'' \end{bmatrix}$$