

B.Tech II Year II Semester (R20) Regular & Supplementary Examinations April/May 2024

DIGITAL LOGIC DESIGN

(Electronics & Communication Engineering)

Time: 3 hours

Max. Marks: 70

PART – A
(Compulsory Question)

- 1 Answer the following: (10 X 02 = 20 Marks)
- | | |
|--------------------------------------------------------------------------|----|
| (a) Convert (615.25_8) to its hexadecimal equivalent. | 2M |
| (b) What are universal gates and why they are called as universal gates? | 2M |
| (c) Compare serial adder and parallel adder. | 2M |
| (d) What do you mean by K-map? Name its advantages and disadvantages? | 2M |
| (e) Differentiate between Latch and flip flop. | 2M |
| (f) What is meant by race around condition in flip-flops? | 2M |
| (g) What is FSM? | 2M |
| (h) What is State assignment? | 2M |
| (i) Write the difference between PLA & PAL. | 2M |
| (j) Differentiate volatile and non-volatile memory. | 2M |

PART – B

(Answer all the questions: 05 X 10 = 50 Marks)

- 2 (a) Convert the following to the corresponding bases 5M
- (i) $(343)_5 = ()_6$; (ii) $(7654)_8 = ()_{10}$
- (iii) Simplify the following Boolean expression to a minimum number of literals $ABC + A'B + ABC'$
- (b) State and prove the following Boolean laws: 5M
- (i) Commutative, (ii) Associative, (iii) Distributive.
- OR**
- 3 (a) Perform the following arithmetic operation using 1's complement method: 5M
- (i) Add $(-19)_{10}$ and $(29)_{10}$; (ii) Add $(21)_{10}$ and $(37)_{10}$
- (iii) Write the truth table and symbols of AND & OR gates.
- (b) Simplify the following expression using Boolean algebra rule $\overline{\overline{AB} + ABC + A(B + AB)}$. 5M
- 4 (a) Simplify the Boolean expression, $F = A' + AB + ABD' + AB'D' + C'$ using Four variable K-Map 5M
- and draw the logic diagram using AOI.
- (b) Implement the following switching function using a Four input multiplexer 5M
- $F(A, B, C, D) = \sum m(0, 1, 2, 4, 6, 9, 10, 13, 14)$.
- OR**
- 5 (a) Reduce the following function using K-Map. 5M
- $F(A, B, C, D, E) = \sum m(1, 4, 8, 10, 11, 20, 22, 24, 25, 26) + d(0, 12, 16, 17)$.
- (b) Design a 4-bit combinational logic to subtract one bit from the other. Draw the logic diagram 5M
- using NAND and NOR Gates.
- 6 (a) Design 4-bit shift register using D flip-flops and explain its working with the help of timing 5M
- diagrams.
- (b) With neat diagram explain the operation of 3-bit universal shift register. 5M

OR

Contd. in Page 2

- 7 (a) Convert SR flip flop into JK Flip-Flop. Draw and explain its logic diagram. 5M
(b) With neat diagram explain the operation of a 3-bit Ripple counter. 5M
- 8 (a) The reduced state table of a sequential machine has 12 rows. What is the minimum number of flip-flops needed to implement the machine? 5M
(b) What is state reduction by partition method? Explain. 5M
- OR**
- 9 (a) How many flipflops are needed to design an FSM with n states using binary encoding for state assignment? Explain FSM capabilities and limitations. 5M
(b) What are the real-life examples of Mealy machines? Differentiate Moore and Mealy. 5M
- 10 (a) Explain the functions and applications of PLAs in memory addressing and implement the following two Boolean functions with a PLA: 5M
 $F1(A, B, C) = \sum (0, 1, 3, 5)$ and $F2(A, B, C) = \sum (1, 2, 4, 7)$
(b) Write Verilog module for a positive edge triggered flip flop with test bench. 5M
- OR**
- 11 (a) Design PAL for a combinational circuit that squares a 3-bit number? 5M
(b) Explain the basic Structure of CPLD and FPGA. 5M

B.Tech II Year II Semester (R20) Regular & Supplementary Examinations August/September 2023

DIGITAL LOGIC DESIGN

(Electronics & Communication Engineering)

Time: 3 hours

Max. Marks: 70

PART – A

(Compulsory Question)

1 Answer the following: (10 X 02 = 20 Marks)

- | | | |
|-----|----------------------------------------------------------------------------------------------------|----|
| (a) | Convert the following numbers with the given radix to decimal. (i) $(4433)_5$ (ii) $(1199)_{12}$. | 2M |
| (b) | What are the three methods of obtaining the 2's complement of a given binary number? | 2M |
| (c) | Multiply out and simplify to obtain a sum of products: $(x' + y + z')(x' + z' + u)(y' + u')$. | 2M |
| (d) | State and prove the De-Morgan's laws. | 2M |
| (e) | What is meant by race around condition in flip-flops? | 2M |
| (f) | Why a multiplexer is called a data selector? Draw the 2x1 MUX. | 2M |
| (g) | Discuss about a serial-in, serial-out shift registers. | 2M |
| (h) | Draw the state diagram of modulo-4 up/down counter. | 2M |
| (i) | State the purpose of reducing the switching functions to minimal form. | 2M |
| (j) | Define full Subtractor. | 2M |

PART – B

(Answer all the questions: 05 X 10 = 50 Marks)

- | | | |
|---|-----------------------------------------------------------------------------------------------------------------------------------|----|
| 2 | (a) Perform the subtraction using 1's complement method.
(i) $11010 - 10000.01$, (ii) $11010 - 1101$, (iii) $101 - 110000$. | 5M |
| | (b) How do you convert a gray number to binary? Generate a 4-bit gray code directly using the mirror image property. | 5M |

OR

- | | | |
|---|-------------------------------------------------------------------------------------------------------------------------------------------------------|----|
| 3 | (a) Convert the following numbers;
(i) $(10101100111.0101)_2$ to Base 10, (ii) $(153.513)_{10}$ to base 8. | 5M |
| | (b) Convert the following to required form.
(i) $(163.789)_{10} = ()_8$, (ii) $(101101110001.00101)_2 = ()_{10}$, (iii) $(292)_{16} = ()_2$. | 5M |
| 4 | (a) Simplify the following using K- map and implement the same using NAND gates. $Y(A, B, C) = \sum(0, 2, 4, 5, 6, 7)$. | 5M |
| | (b) Obtain the simplified expression in SOP form of:
$F(a, b, c, d, e) = \sum(1, 2, 4, 7, 12, 14, 15, 24, 27, 29, 30, 31)$ using K-map. | 5M |

OR

- | | | |
|---|---------------------------------------------------------------------------------------------------------------------------------------------------------------------------|----|
| 5 | (a) Reduce the following expression to the simplest possible POS and SOP forms. $F = \sum m(6, 8, 13, 18, 19, 25, 27, 29, 31) + d(2, 3, 11, 15, 17, 24, 28)$. | 5M |
| | (b) State and prove consensus theorem? Solve the given expression using consensus theorem.
(i) $AB + AC + BC + BC + AB$, (ii) $(A + B)(A + C)(B + C)(A + D)(B + D)$. | 5M |
| 6 | (a) Write the differences between ring counter to johnson counter. | 5M |
| | (b) Design a combinational circuit for a 2-bit magnitude comparator. | 5M |

OR

- | | | |
|---|-----------------------------------------|----|
| 7 | (a) Design a 4-bit ring counter. | 5M |
| | (b) Draw and design the decade counter. | 5M |

Contd. in Page 2

- 8 (a) Write the capabilities and limitations of FSM. 5M
(b) Convert a D flip flop into SR flip flop and JK flip flop. 5M
OR
- 9 (a) Explain the types of FSM. 5M
(b) Explain the mealy to more conversion with an example. 5M
- 10 (a) Write the design of Sequential circuits using ROMs. 5M
(b) Explain about (i) conditional operator, (ii) if-else statement in verilog. 5M
OR
- 11 (a) Write the advantages of FPGAs. 5M
(b) Explain the for loop using storage elements with CAD tools. 5M
