

B.Tech II Year I Semester (R20) Supplementary Examinations August/September 2023

DIGITAL ELECTRONICS & MICROPROCESSORS

(Common to CSE (Cyber Security), IT, CSE, CSE (AI), CSE (AI&ML), AI&DS, CSE (IoT), CSE (DS), and AI&ML)

Time: 3 hours

Max. Marks: 70

PART – A
(Compulsory Question)

- 1 Answer the following: (10 X 02 = 20 Marks)
- | | |
|--|----|
| (a) Realise OR gate using NAND gates. | 2M |
| (b) State the limitations of K-maps. | 2M |
| (c) Is the PAL same as the PLA? Justify. | 2M |
| (d) Compare and contrast Encoder and Multiplexers. | 2M |
| (e) What is triggering? What is the need for trigger in a flip-flop? | 2M |
| (f) Compare asynchronous and synchronous counters. | 2M |
| (g) What is pipelined architecture? | 2M |
| (h) What is the function of D flag in 8086? | 2M |
| (i) Give an importance of the assembler directive EVEN. | 2M |
| (j) What are the flags available in 8051? | 2M |

PART – B

(Answer all the questions: 05 X 10 = 50 Marks)

- 2 (a) Convert $(19.625)_{10}$ to binary and octal number systems. 5M
 (b) Implement the following Boolean function with NAND gates 5M
 $F(x, y, z) = \sum m(1, 2, 3, 4, 5, 7).$
- OR**
- 3 Simplify the expression using K map technique. 10M
 $F = \sum m(0, 2, 4, 5, 6, 7, 8, 10, 11, 12, 14, 15).$
- 4 (a) Design a half subtractor circuit. 5M
 (b) Design and explain the working of full adder. 5M
- OR**
- 5 Design a 3 to 8 line decoder with necessary diagram. 10M
- 6 Design and explain the working of an up-down ripple counter. 10M
- OR**
- 7 Explain the operation of serial in parallel out shift register. 10M
- 8 Name and explain about the different addressing modes used in 8086 with suitable examples. 10M
- OR**
- 9 Explain the interrupts of 8086 in detail. 10M
- 10 Give the operation of the following 8086 instructions. 10M
 (i) ADC, (ii) DEC, (iii) MUL, (iv) XOR.
- OR**
- 11 Explain about the different addressing modes supported by 8051 microcontroller. 10M

B.Tech II Year I Semester (R20) Supplementary Examinations April/May 2024

DIGITAL ELECTRONICS & MICROPROCESSORS

(Common to CS&IT, IT, AI&DS, CSE(AI), CSE(DS), CSE(AI&ML), CSE(IoT), CSE(CS), CSE and AI&ML)

Time: 3 hours

Max. Marks: 70

PART – A
(Compulsory Question)

- 1 Answer the following: (10 X 02 = 20 Marks)
- | | |
|---|----|
| (a) State De-Morgan's theorem. | 2M |
| (b) Define 'Minterm' and 'Maxterm'. | 2M |
| (c) State the concept of parallel binary adder. | 2M |
| (d) Identify the function of select inputs of a MUX. | 2M |
| (e) What is the primary drawback of an RS flip-flop, and how it overcomes using clocked RS flip-flop? | 2M |
| (f) Differentiate between a JK flip-flop and a D flip-flop in terms of their functionality. | 2M |
| (g) Compare Min and Max modes of 8086. | 2M |
| (h) List the flags present in the 8086 processor. | 2M |
| (i) What is an Assembler directive? | 2M |
| (j) Define Microcontroller. | 2M |

PART – B
(Answer all the questions: 05 X 10 = 50 Marks)

- 2 Simplify the following function using five variable mapping;
F = (8, 9, 10, 11, 13, 15, 16, 18, 21, 24, 25, 26, 27, 30, 31). 10M
- OR**
- 3 Explain the different types of codes and conversions with your own example. 10M
- 4 Draw and explain the working of 4 bit adder – subtractor circuit. 10M
- OR**
- 5 Implement the following function with a Multiplexer
f (a, b, c, d) = Σ (0, 1, 3, 4, 8, 9, 15). 10M
- 6 Describe the operation of universal shift register with neat block diagram. 10M
- OR**
- 7 Explain the operation of a BCD ripple counter and provide a detailed explanation along with a timing diagram to illustrate its functioning. 10M
- 8 Describe the internal architecture of 8086 Microprocessor with neat diagrams. 10M
- OR**
- 9 Explain the pin diagram of 8086 Microprocessor. 10M
- 10 Explain the instruction set of 8086 processor with examples. 10M
- OR**
- 11 Write an ALP to compute multiplication of two 8 bit numbers and store it in memory location using 8051 instruction set. 10M
